

**International University of Ecuador**  
**Faculty of Technical Sciences**

SCHOOL OF MECATRONICS ENGINEERING

INDUSTRIAL AUTOMATIZATION

*Lab's preparatory No 3: Timer conector*

Author:  
Pablo Guacho  
Sebastian Osorio

Sep 20222 - Jan 2023

# Lab's preparatory No 3 \*

Sebastian Osorio<sup>1</sup>[0000-0003-0106-5482] and Pablo Guacho<sup>1</sup>

International University of Ecuador, Quito Av. Jorge Fernández and Av. Simón Bolívar 170201, Ecuador [seosoriogu@uide.edu.ec](mailto:seosoriogu@uide.edu.ec) <https://www.uide.edu.ec/>

## 1 Timer AH3-AB

Some of the basic characteristics of the timer AH3-AB are:

1. Exclusive CMOS IC assures high performance stability, and accuracy.
2. High repeat accuracy  $\pm 1\%$ .
3. Short resetting time-100 msec. ax.
4. Wide variety of type-14 time ranges.(0.1 sec. to 10 hrs)
5. 2 modes selectable via slide switch: Mode A(2C) for DPDT time-limiting output contacts and Mode B(1A1C) for SPDT instantaneous and time-limiting output contacts

Table 1: Multi range timer AH3-AB specifications.

AH3-AB Specifications	
Rated voltage	AC 110V, 220V, 380V, 440V DC 12V, 24V
Rated frequency	50/60Hz
Operating voltage	AC 85-110% of rated voltage DC 80-110% of rated voltage
Consumed power	2VA for AC / About 2W for DC
Control method	Time-limit operation / Self-resetting
Contact rating	250V AC 10A (P.F.=1)
Ambient temp.	-10°C ~+55°C
Ambient humidity	45~85% RH

---

\* UIDE x.

Fig. 1. Connection Diagram



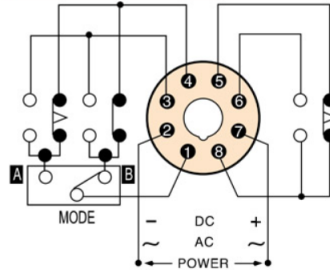
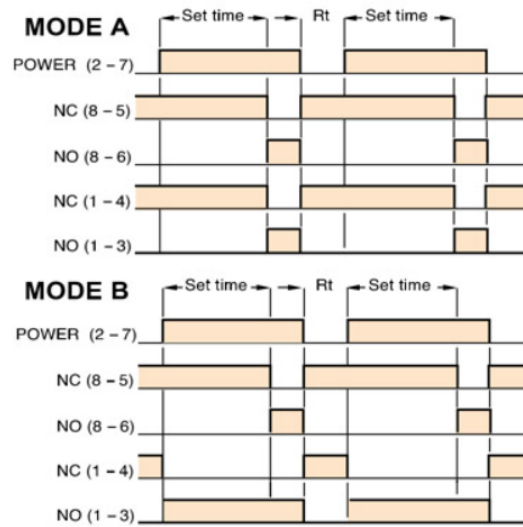


Fig. 2. Modes operation Chart

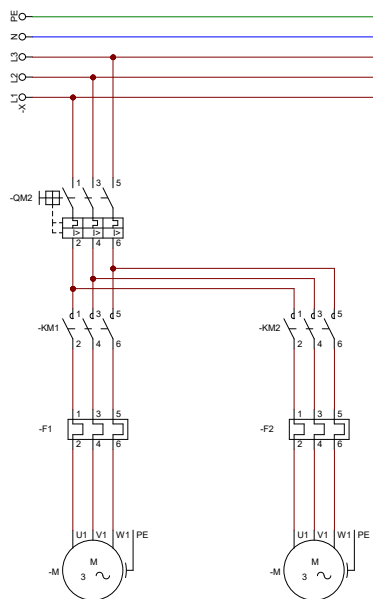

## 2 Circuit proposed

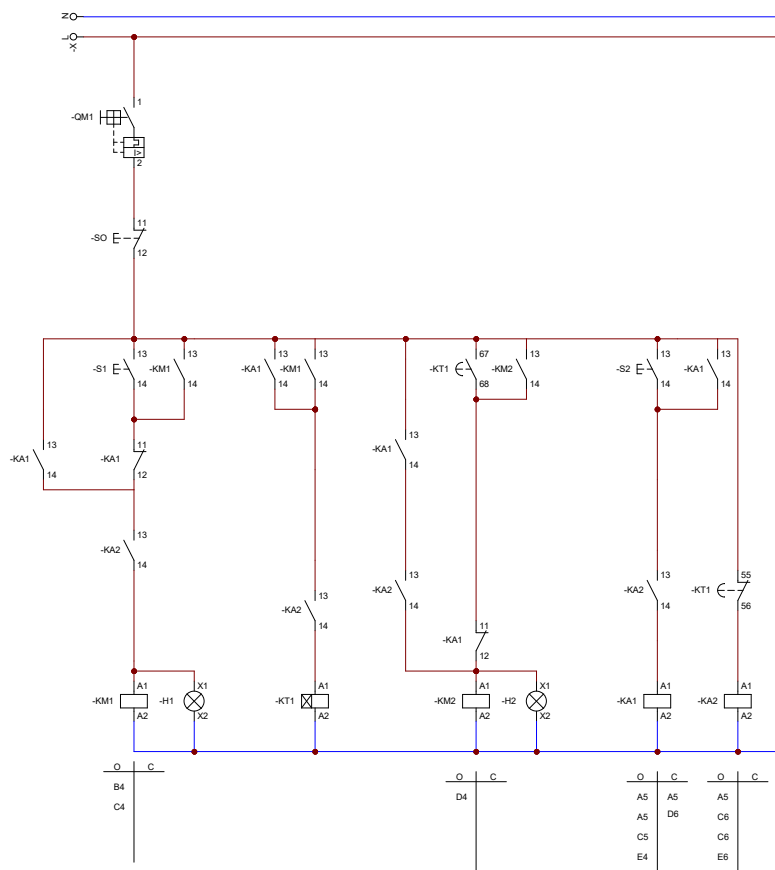1. When button S1 is pressed (momentarily), KM1 must be turned on and after a time  $t_1$ , contactor KM2 will turn on and KM1 will turn off.
2. If button S2 is pressed (momentarily), contactor KM1 and contactor KM2 will turn on, and after a time  $t_1$ , KM1 will turn off.
3. Additionally, the circuit will have an emergency stop button S0, which will stop the operation of the fans at any time.
4. Include a lamp that indicates the operation of each fan.
5. The design must use a timed relay (ON DELAY) and optimize the design with the least number of contactor and contacts.



Drawn	Date	Name	Signature	Designed by	Título	Date	Page
Drawn	23-10-2022	GUACHO P		UIDE	PREPARATORY 3	23-Oct-2022	1 de 1
Drawn	25-10-2022	OSORIO S				File:	LAB3_GuachoOsorio.