

**International University of Ecuador**  
**Faculty of Technical Sciences**

SCHOOL OF MECATRONICS ENGINEERING

INDUSTRIAL AUTOMATIZATION

*Lab's Preparatory No 2:*

Authors:  
Sebastian Osorio  
Pablo Guacho

Sep 20222 - Jan 2023

# Lab's preparatory No. 2\*

Sebastian Osorio<sup>1</sup>[0000–0003–0106–5482] and Pablo Guacho<sup>1</sup>[0000–0003–0106–5482]

International University of Ecuador, Quito Av. Jorge Fernández and Av. Simón  
Bolívar 170201, Ecuador [uide@uide.edu.ec](mailto:uide@uide.edu.ec) <https://www.uide.edu.ec/>

## 1 Instructions

Design the control circuit that performs the operating sequence of three three-phase motors (M1, M2 and M3). The components are the following:

- switch to activate the control circuit.
- Two Normally Open push buttons S1 and S2.
- Two Normally Closed push buttons S01 and S02.
- Three contactors KM1, KM2 and KM3 for the control of motors M1, M2 and M3.
- Two contactors KA1 and KA2 to control two lamps H1 and H2, respectively.

### 1.1 Operating sequence

The operating sequence of the circuit is as follows:

- Pressing button (S1) activates motor M1.
- Pressing button (S2) activates motor M2 and M3.
- Pressing button (S01) causes the general system shutdown (all components are deactivated).
- Pressing button momentarily (S02) deactivates motor M3, that is, as long as the button is kept pressed. Operating sequence of lamp H1 (KA1), it is activated in the following cases:
  - When motor M1 (with S1) and motors M2 and M3 (with S2) are activated. Operating sequence of lamp H2 (KA2), it is activated in the following cases:
  - When motor M2 and M3 are activated (with S2) and if motor M1 is OFF.
  - When motor M1 is ON (with S1) and motors M2 and M3 are OFF.
  - If motor M3 is ON, when S02 button is kept pressed, motor M3 turns OFF. If S02 button is released, the M3 motor continues to be activated.

---


\* UIDE.

## 2 Circuit diagram

Considering all the needs of the circuit, the following diagram is proposed:

### 2.1 Power circuit

Fig. 1. Power circuit, used to control the motors

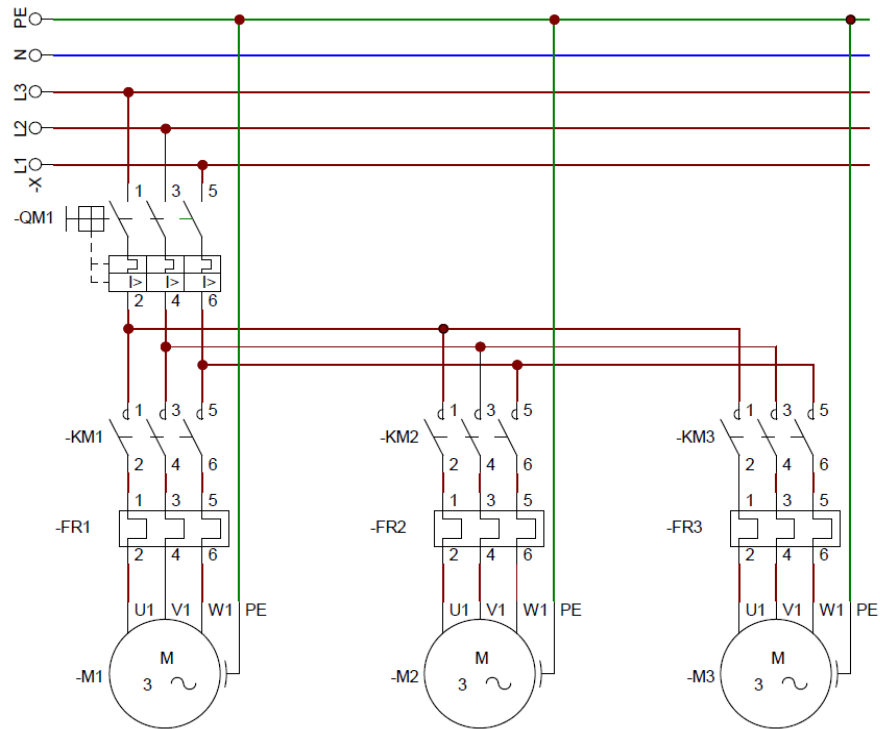

## 2.2 Control circuit

Fig. 2. Insert caption

